



**L-Università
ta' Malta**

MATRICULATION AND SECONDARY EDUCATION CERTIFICATE
EXAMINATIONS BOARD

**SECONDARY EDUCATION CERTIFICATE LEVEL
2022 MAIN SESSION**

SUBJECT:	Engineering Technology
PAPER NUMBER:	Controlled – Unit 2
DATE:	20 th May 2021
TIME:	10:00 a.m. to 11:35 a.m.

Name of candidate _____

I.D. number _____

School _____

Class _____

Answer **ALL** questions in the space provided.

Scenario

- An electronics technician working in an engineering company is required to read and interpret circuit diagrams.
- The technician is required to assemble, and test simple circuits built on various prototype boards.

Question 1

K-1 (4 marks)

Materials are normally classified according to their electrical properties as conductors, semi-conductors or insulators.

a) Categorise the following materials as insulators or conductors.

- i) Copper: _____ (0.25)
- ii) Wood: _____ (0.25)
- iii) Ceramic: _____ (0.25)
- iv) Iron: _____ (0.25)

b) Define the term semiconductor.

(1)

c) State **TWO** parameters affecting the resistance of a wire.

Parameter 1: _____

Parameter 2: _____

(2)

Question 2

K-3 (4 marks)

An electrical circuit provides a path around which electricity can flow.

- a) Differentiate between an open circuit and a closed circuit.

(1)

- b) **THREE** 1.5V batteries connected in series are used to power **TWO** light bulbs connected in parallel when a switch is closed. Draw the described circuit in the space provided.

(1)

- c) Identify (by marking and labelling) **TWO** series and **ONE** parallel sub-circuits on the circuit shown in Figure 2 below.

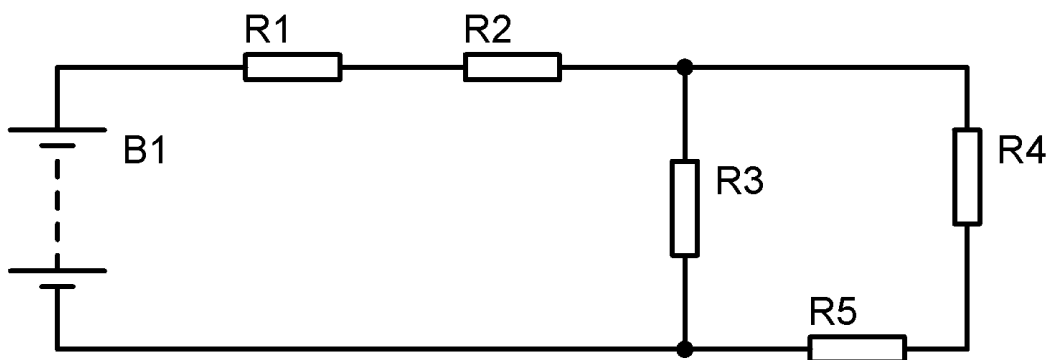


Figure 2 - Series-parallel circuit.

(2)

Please turn the page.

Question 3

C-2 (6 marks)

Resistors can be connected in various series and parallel combinations to form resistive circuits.

a) Find the total resistance of the circuit shown in figure 3 below. Show all your working.

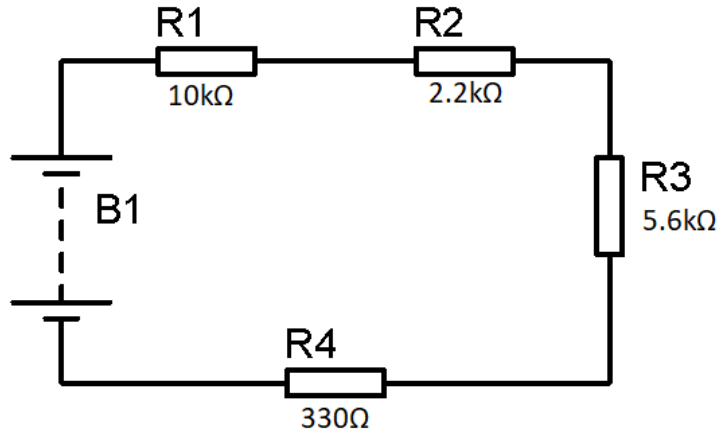


Figure 3 – Circuit 1.

(2)

b) Find the total resistance of the circuit shown in Figure 4 below. Show all your working.

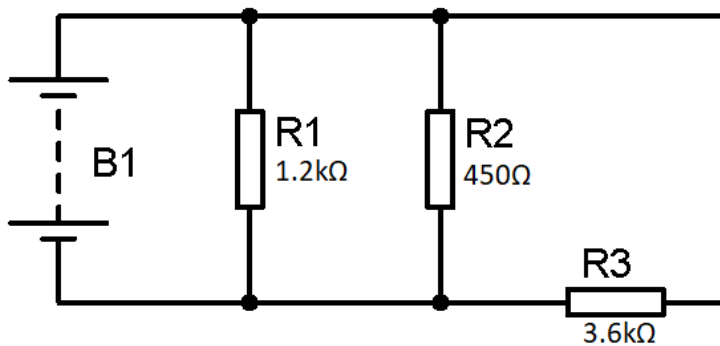


Figure 4 – Circuit 2.

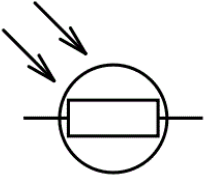
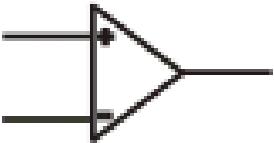



Question 4

K-9 (4 marks)

Components are represented in circuit diagrams using standard symbols.

a) Identify the electronic symbols by completing Table 1 below.

Table 1 – Electronic Symbols.

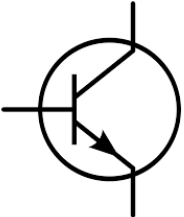	Electronic Symbol	Name
i)		_____ (0.2)
ii)		_____ (0.2)
iii)		_____ (0.2)
iv)		_____ (0.2)
v)		_____ (0.2)

(Source: <https://www.electrical4u.com/electrical-international-symbol/>)





b) Match the following SI units to their respective parameters by drawing a line between them.

i) Volts	Current
ii) Amps	Resistance
iii) Farads	Voltage
iv) Ohms	Capacitance
v) Watts	Power

(1)

c) Table 2 below shows different packaging for capacitors and resistors. Identify each of the given packaging, by underlining the correct answer.

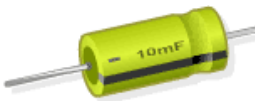Table 2 – Component Packaging.

	Component	Packaging 1	Packaging 2
i)	Capacitor	 Radial / Axial	 Radial / Axial
ii)	Resistor	 Through hole / Surface mount	 Through hole / Surface mount

(Source: <https://www.antiqueradios.com/>)
 (Source: <http://www.spazztech.net/resistors.html>)

(2)

Please turn the page.





Question 5

K-10 (4 marks)

Different tools are required to construct electronic circuits.

a) Label the following tools by completing Table 3 below.

Table 3 – Tools.

	Tool	Name
i)		_____ (0.25)
ii)		_____ (0.25)
iii)		_____ (0.25)
iv)		_____ (0.25)

Source: <https://makeradvisor.com/how-to-set-up-an-electronics-lab-tools-and-equipment/>

b) Identify **FIVE** steps which are required to use a soldering iron effectively.

Step 1: _____

Step 2: _____

Step 3: _____

Step 4: _____

Step 5: _____

(1)

c) Outline the function of each of the following tools used to construct a circuit on a PCB.

De-soldering pump

(1)

This question continues on the next page.

PCB driller

(1)

Blank Page

Blank Page