



L-Università
ta' Malta

MATRICULATION AND SECONDARY EDUCATION CERTIFICATE
EXAMINATIONS BOARD

**SECONDARY EDUCATION CERTIFICATE LEVEL
2021 SUPPLEMENTARY SESSION**

SUBJECT:	Engineering Technology
PAPER NUMBER:	Synoptic – Unit 2
DATE:	3 rd November 2021
TIME:	4:00 p.m. to 6:05 p.m.

**THIS PAPER SHOULD BE RETURNED TO THE INVIGILATOR
AFTER THE EXAMINATION.**

Answer **ALL** questions in the space provided. The use of non-programmable electronic calculators is allowed.

Scenario

- An engineering company which specialises in manufacturing integrated circuits has a vacancy for a technician.
- As part of the selection process, applicants are given the following test to assess their knowledge in electronics and demonstrate that they are suitable for the job.

Question 1

K-1 (6 marks)

a. Categorise the following materials as insulators or conductors by filling in Table 1 below.

Aluminium	Brass	Ceramic	Glass	Gold
Iron	Paper	Plastic	Steel	Wood

Table 1 – Conductors or Insulators.

Conductors	Insulators

(2)

b. Define the term semi-conductor.

(2)

c. State **TWO** parameters affecting resistance of a material.





_____ (2)

Question 2

K-4 (8 marks)

a. Identify the different designs of switches given in Table 2 below.

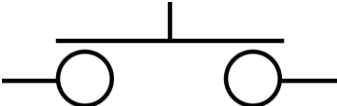
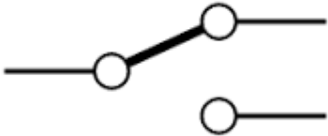

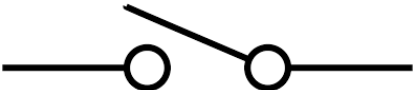
Table 2 – Different designs of switches.

	Switch	Name of Switch
i.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
ii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iv.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>

This question continues on next page.

b. Identify the different types of switches from their schematics in terms of poles and throws, shown in Table 3.

Table 3 – Different types of switches.

	Schematic symbol	Type of Switch
i.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
ii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iv.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>

c. Select the appropriate switch for the two scenarios given below. Each scenario requires a different type of switch.

i. Select a switch for an emergency button in a classroom. The electricity in the classroom is normally on. During an emergency, the switch is pressed to stop the flow of electricity.

_____ (2)

ii. Select a switch which turns the power of a wireless mouse on or off.




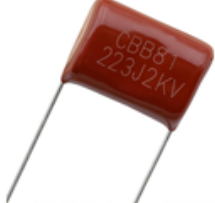
_____ (2)

Question 3

K-5 (8 marks)

a. Identify the different types of capacitors provided in Table 4.

Table 4 – Different types of capacitors.

	Picture of Capacitor	Name the type of capacitor
i.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
ii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>
iv.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.5)</p>

This question continues on next page.


b. Rank the given values of capacitors in order, starting from the smallest to the largest value.

$47000\eta F$, $33000pF$, $220\mu F$, $1000\mu F$, $15\eta F$, $47000\eta F$, $1\mu F$, $100\eta F$, $20pF$


- i. Smallest: _____ (0.25)
- ii. _____ (0.25)
- iii. _____ (0.25)
- iv. _____ (0.25)
- v. _____ (0.25)
- vi. _____ (0.25)
- vii. _____ (0.25)
- viii. Largest: _____ (0.25)

c. On the graphs provided, sketch the voltage-time graphs of a charging and discharging capacitor.

Charging

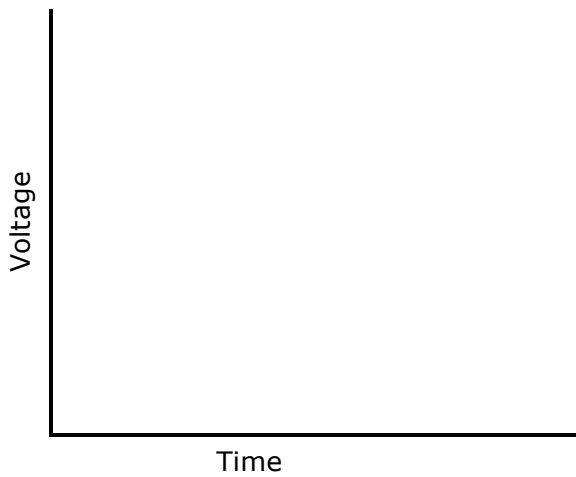

Discharging

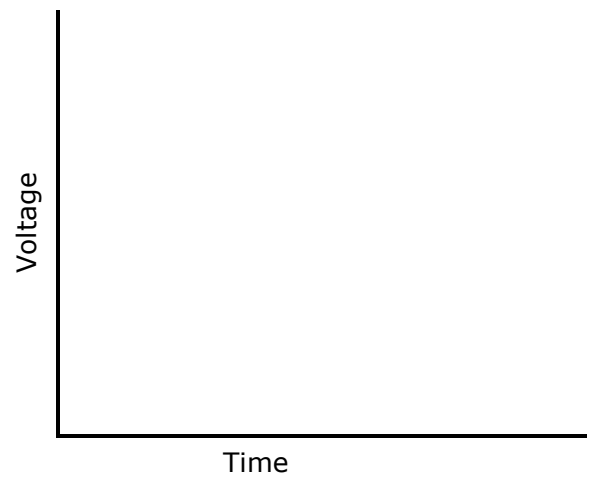

(4)

Question 4

K-7 (8 marks)

a. List **TWO** analogue devices.

Analogue Device 1: _____ (1)

Analogue Device 2: _____ (1)

b. i. List **ONE** semiconductor material which is used in the component of Figure 1.

_____ (0.4)

ii. List the name of lead a and lead b.



Figure 1

(0.4)

iii. List **ONE** semiconductor material which is used in the component in Figure 2.

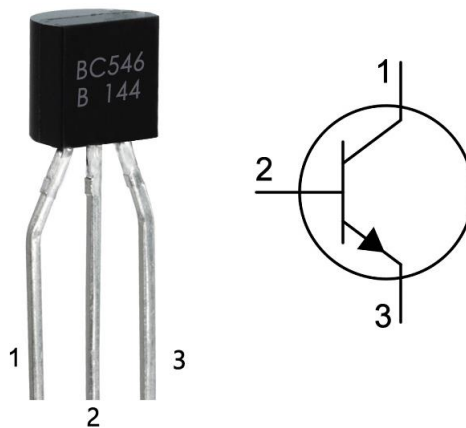


Figure 2

_____ (0.4)



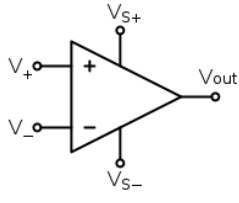
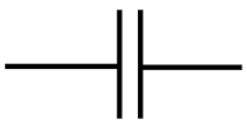
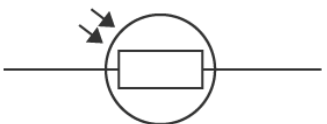
This question continues on next page.

Question 5

K-9 (8 marks)

a. Identify the electronic symbols given in Table 5 below.

Table 5 – Electronic symbols.

	Symbols	Name of electronic component
i.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
ii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
iii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
iv.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
v.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>

This question continues on next page.

b. Match the SI units to their respective parameters by drawing a line between Column A and Column B.

Column A (SI Unit)

Amps

Farads

Volts

Ohms

Watts

Column A (Parameter)

Capacitance

Current


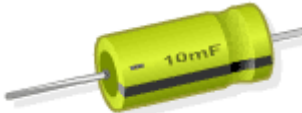


Power

Voltage

Resistance

(2)

c. Identify different packaging of the following electronic components by underlining the correct answer under the given component.

<p>Capacitor</p>	 <p>Source: https://www.google.com/ Radial or Axial</p>	 <p>Source: https://www.google.com/ Radial or Axial</p>
<p>Resistor</p>	 <p>Source: https://www.google.com/ Through hole or Surface Mount</p>	 <p>Source: https://www.google.com/ Through hole or Surface Mount</p>






(4)

Question 6

K-10 (8 marks)

a. Label the different tools used in electronic circuit construction given in Table 6.

Table 6 – Tools for circuit construction.

	Tools	Name of tool
i.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
ii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
iii.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
iv.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>
v.	 <p>Source: https://www.google.com/</p>	<p>_____</p> <p>(0.4)</p>

Question 7

C-2 (12 marks)

a. Find the total resistance of the circuit shown in Figure 3. Show all your workings.

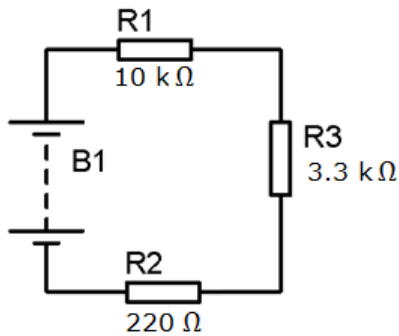


Figure 3 – Circuit 1

(4)

b. Find the total resistance of the circuit shown in Figure 4. Show all your workings.

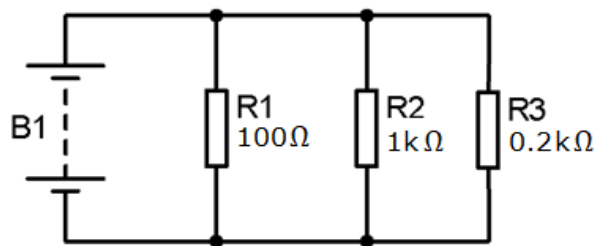


Figure 4 – Circuit 2

(4)

This question continues on next page.

Question 8

C-4 (12 marks)

a. 'AND' and 'NOR' are types of logic gates. List **FOUR** other different logic gates and their respective symbols by completing Table 7.

Table 7 – Logic gates and their symbols.

	Logic Gate Name	Logic Gate Symbol
i.	_____	(1)
ii.	_____	(1)
iii.	_____	(1)
iv.	_____	(1)

b. Write the truth table of the following logic gates given in Table 8.

Table 8 – Logic gates and their truth tables.

Logic Gate	Logic Gate Truth Table		
AND Gate	Inputs		Output
	A	B	Y
	0	0	
	0	1	
	1	0	
	1	1	

This question continues on next page.

NOR Gate	Inputs		Output
	A	B	Y
	0	0	
	0	1	
	1	0	
	1	1	

(2)

c. Figure 6 shows the same circuit but with different logic inputs. Determine the output of the circuit shown below by filling in the boxes after each logic gate.

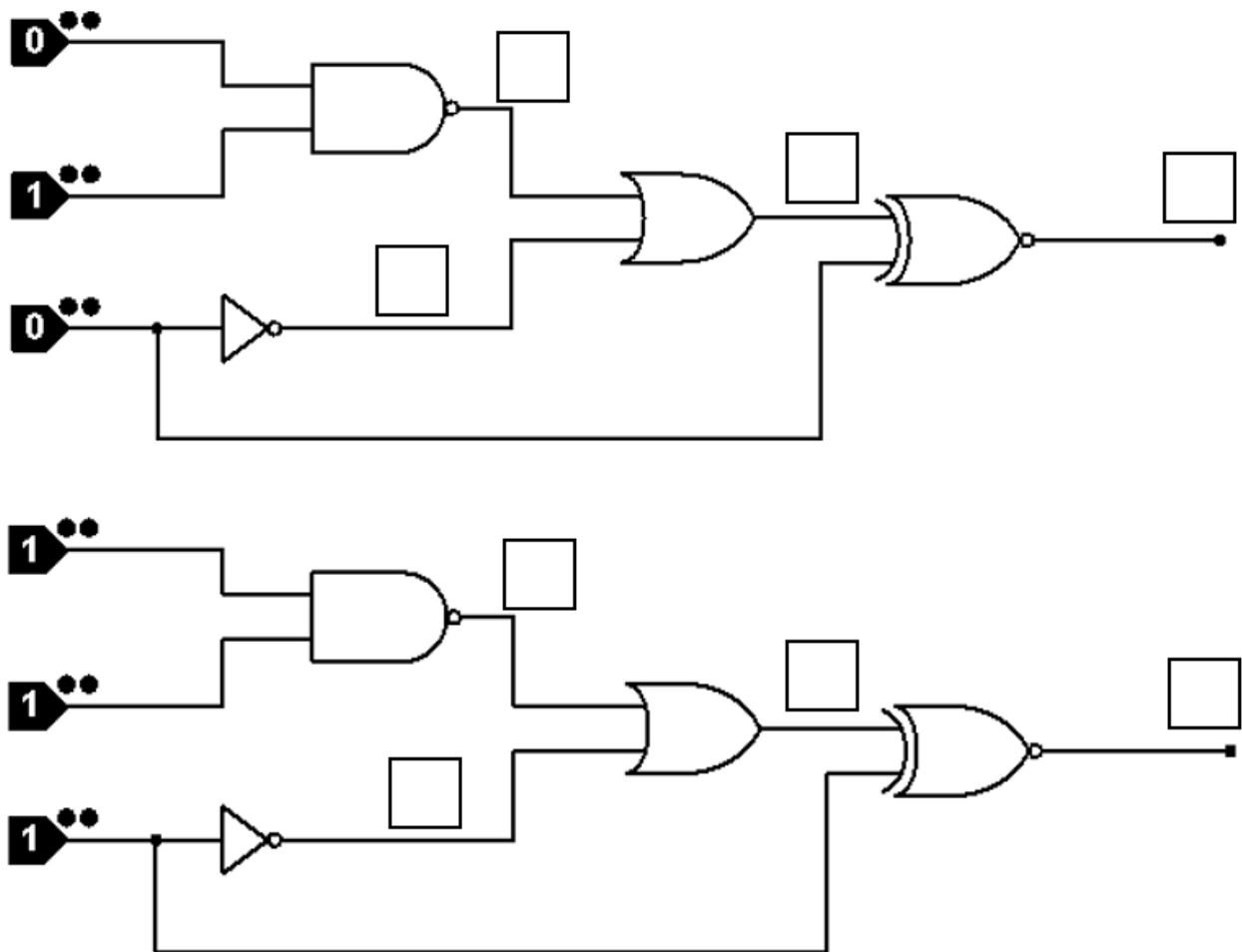


Figure 6 – Logic Circuit

(4)